

# Circuitos RF

## Gustavo Soares


2020/1

### PRELIMINAR 1

#### 1) Equações Pseudo Power-Waves

#### 2) Quadripolo

$$L = 1 \mu H$$

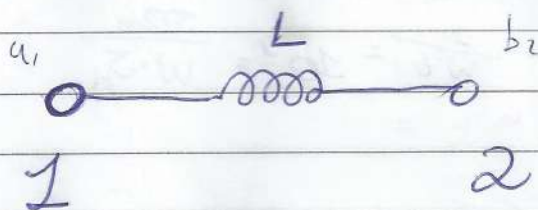


$$Z_L = j\omega L$$

$$3) a_1 = \frac{V_1 + I_2 \cdot Z_0}{2 \cdot \sqrt{Z_0}} = \frac{V_{a1}}{\sqrt{Z_0}}$$

$$a_2 = \frac{V_2 + I_2 \cdot Z_0}{2 \cdot \sqrt{Z_0}} = \frac{V_{a2}}{\sqrt{Z_0}}$$

$$b_1 = \frac{V_1 - I_2 \cdot Z_0}{2 \cdot \sqrt{Z_0}} = \frac{V_{b1}}{\sqrt{Z_0}}$$
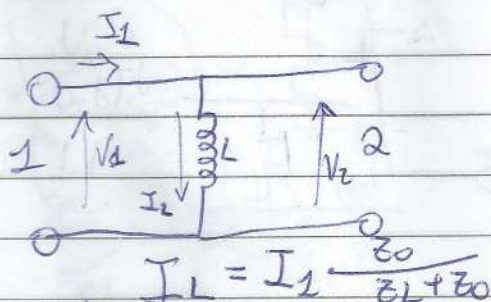
$$b_2 = \frac{V_2 - I_2 \cdot Z_0}{2 \cdot \sqrt{Z_0}} = \frac{V_{b2}}{\sqrt{Z_0}}$$



$$I_L = I_1 \cdot \frac{Z_0}{Z_L + Z_0}$$

$$V_1 = Z_L \cdot I_L$$

$$V_2 = V_1$$

Para o indutor em paralelo:

$$\Rightarrow S_{11} = \frac{b_1}{a_1} \Big|_{a_2=0}$$

$$\begin{aligned} \Rightarrow S_{11} &= \frac{V_1 - I_2 \cdot Z_0}{V_1 + I_2 \cdot Z_0} \\ &= \frac{(Z_0 \cdot Z_L / (Z_0 + Z_L)) - Z_0}{(Z_0 \cdot Z_L / (Z_0 + Z_L)) + Z_0} \\ &= \frac{-Z_0^2}{2Z_L Z_0 + Z_0^2} \\ &= \frac{-Z_0}{2Z_L + Z_0} = \frac{-1}{2 \frac{Z_L}{Z_0} + 1} \end{aligned}$$

$$\Rightarrow S_{21} = \frac{b_2}{a_1} \Big|_{a_2=0} = \frac{V_2 - I_2 \cdot Z_0}{V_1 + I_2 \cdot Z_0}$$

$$\Rightarrow S_{21} = \frac{-I_2 \cdot Z_0 - I_2 \cdot Z_0}{I_1 \cdot \left[ \left( \frac{Z_L \cdot Z_0}{Z_L + Z_0} \right) + Z_0 \right]}$$

$$= -2 \cdot I_1 \cdot \left( \frac{Z_0}{Z_L + Z_0} - 1 \right) \cdot Z_0$$

$$I_1 \cdot \left[ \left( \frac{Z_L \cdot Z_0}{Z_L + Z_0} \right) + Z_0 \right]$$

$$= \frac{-2Z_0^2 / (Z_L + Z_0) + 2Z_0}{Z_L \cdot Z_0 / (Z_L + Z_0) + Z_0}$$



$$\Rightarrow S_{21} = \frac{-2 \cdot Z_0 / Z_L + 2 \cdot (Z_L + Z_0) / Z_L}{1 + \frac{Z_L + Z_0}{Z_L}} = \frac{2}{2 + Z_0 / Z_L}$$

Como REDE É RECÍPROCA:  $S_{21} = S_{12}$

Como REDE É SÍMÉTRICA:  $S_{11} = S_{22}$

$$4) S_{11} = S_{22} = \frac{-1}{2 \cdot \frac{Z_L}{Z_0} + 1} = \frac{-1}{2 \cdot \frac{j \cdot 2\pi \cdot 900 \cdot 10^6 \cdot 20^{-9}}{50} + 1}$$

$f = 900 \text{ MHz}$   
 $Z_0 = 50 \Omega$   
 $L = 20 \text{ nH}$

$$= -0,95 + j0,21$$

$$= 0,975 \angle 2,919^\circ \text{ rad}$$

$$= 0,975 \angle 167,25^\circ$$

$$S_{21} = S_{12} = \frac{2}{2 + \frac{Z_0}{Z_L}} = \frac{2}{2 + \frac{50}{j \cdot 2\pi \cdot 900 \cdot 10^6 \cdot 20^{-9}}}$$

$$= 0,0487 + j0,215$$

$$= 0,221 \angle 1,35^\circ \text{ rad}$$

$$= 0,221 \angle 77,25^\circ$$

Logo:  $S = \begin{bmatrix} 0,975 \angle 167,25^\circ & 0,221 \angle 77,25^\circ \\ 0,221 \angle 77,25^\circ & 0,975 \angle 167,25^\circ \end{bmatrix}$