

Circuitos RF - EEL7319

Gustavo Simões

RF Design Vol. 3 (Michael/Steve)

5.16

1)  $R_{in}$  deve ser  $5 \Omega$  (para máxima transferência de potência)

$$\text{Logo: } R_{in} = \frac{V_z^2}{I_z^2} = \left(\frac{m}{n}\right)^2 \cdot 2 \cdot R_0$$

$$\Rightarrow 5 = \left(\frac{m}{n}\right)^2 \cdot 2 \cdot 75 \Rightarrow \frac{m}{n} = 0,1825$$

$$2) Q = \omega_r \cdot L / R$$

$$L = 10 \text{ nH}$$


$$R = 5 \Omega$$

$$f = 1 \text{ GHz}$$

$$= 2\pi \cdot 10^9 \cdot 10 \cdot 10^{-9} / 5$$

$$= 12,56$$


7)

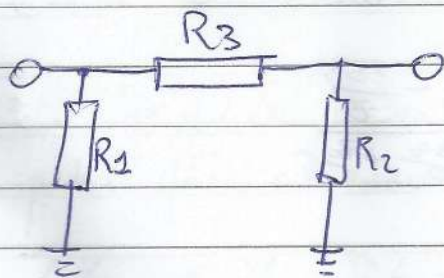

$$R_1 = R_2$$

$$Z_0 = \sqrt{(R_1^2 \cdot R_3) / (2R_1 + R_3)}$$

$$K = \sqrt{(R_1 + Z_0) / (R_1 - Z_0)}$$

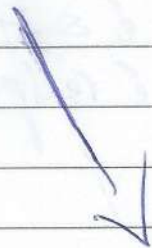

$$\Rightarrow R_1 = \frac{Z_{01} \cdot (K-1) \cdot \sqrt{Z_{02}}}{(K+1) \cdot \sqrt{Z_{02}} - 2 \cdot \sqrt{K \cdot Z_{01}}}$$

$$\text{Como } Z_{01} = Z_{02} = Z_0$$

$$\text{Então:}$$

$$\Rightarrow R_2 = \frac{Z_{02} \cdot (K-1) \cdot \sqrt{Z_{01}}}{(K+1) \cdot \sqrt{Z_{01}} - 2 \cdot \sqrt{K \cdot Z_{02}}}$$

$$R_1 = R_2 = Z_0 \cdot \left( \frac{\sqrt{K} + 1}{\sqrt{K} - 1} \right)$$

$$\Rightarrow R_3 = \frac{(K-1)}{2} \cdot \sqrt{\frac{Z_{01} \cdot Z_{02}}{K}}$$

$$\text{e}$$

$$R_3 = \frac{Z_0 \cdot (K-1)}{2 \cdot \sqrt{K}}$$

Se  $R_1 = R_2$  então:

$$\Rightarrow Z_0 = \sqrt{\frac{R_1^2 \cdot R_3}{2 \cdot R_1 + R_3}} \quad \text{e} \quad K = \left( \frac{R_1 + Z_0}{R_1 - Z_0} \right)^2$$



# 8) Resistive Pi Attenuator

TI-network

$$K_{dB} = 10 \log(K)$$

$$\Rightarrow K = 10^{20/10} = 10$$

$$K_{dB} = 10 \text{ dB}$$

$$Z_0 = 100 \Omega$$



$$\Rightarrow R_1 = R_2 = Z_0 \cdot \left( \frac{\sqrt{K} + 1}{\sqrt{K} - 1} \right)$$

$$= 100 \cdot (\sqrt{10} + 1) / (\sqrt{10} - 1)$$

$$= 192,5 \Omega$$

$$\Rightarrow Z_0 = \sqrt{\frac{R_1^2 \cdot R_3}{2R_1 + R_3}}$$
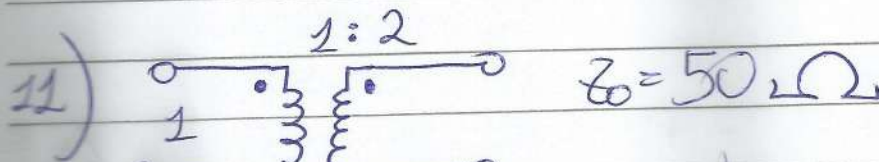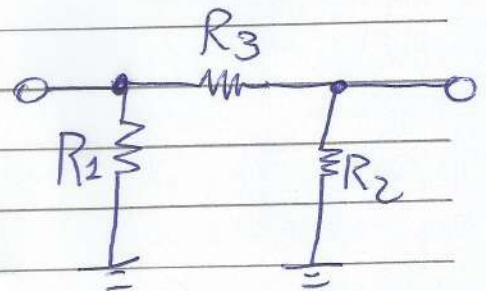
$$\Rightarrow R_3 = \frac{Z_0^2 \cdot 2R_1}{(R_1^2 - Z_0^2)} = 142,30 \Omega$$



Pelos parâmetros ABCD tabelados:

$$\Rightarrow A = n = 0,5$$

$$\Rightarrow B = 0$$

$$\Rightarrow C = 0$$

$$\Rightarrow D = 1/n = 2$$

$$\Rightarrow \Delta = A + B/Z_0 + C \cdot Z_0 + D = 2,5$$

$$\Rightarrow S_{11} = \frac{A + B/Z_0 - C \cdot Z_0 - D}{\Delta}$$

$$= -4,5 / 2,5 = -0,6$$

$$\Rightarrow S_{12} = \frac{2 \cdot (AD - BC)}{\Delta}$$

$$= 2 / 2,5 = 0,8$$

$$\Rightarrow S_{21} = \frac{2}{\Delta} = \frac{2}{2,5} = 0,8 = S_{12}$$

$$\Rightarrow S_{22} = \frac{-A + B/Z_0 - C \cdot Z_0 + D}{\Delta}$$

$$= 1,5 / 2,5 = 0,6$$

$$S = \begin{bmatrix} -0,6 & 0,8 \\ 0,8 & 0,6 \end{bmatrix}$$