

[Resultado do Simulador verificado]

Gustavo Simas

EEL7319 - Circuitos RF

Seção 6.12

$$1) R_o = 3 \, \Omega \quad a) R_{in} = n^2 \cdot R_L \Rightarrow n = \sqrt{\frac{R_{in}}{R_L}} = \sqrt{\frac{3}{50}} \approx 0,245$$

$$R_L = 50 \, \Omega$$

$$b) \text{Reflection Coef. } \Gamma_{in} = S_{11} = \frac{n^2 - 1}{n^2 + 1} = -0,8868$$

$$c) R_{L_{dB}} = -20 \log |\Gamma_{in}| = -20 \log(0,8868) = 1,0435 \, \text{dB}$$

$$d) m_2 = 100 \Rightarrow m_1 = \sqrt{\frac{3}{50}} \cdot 100 \approx 25 \text{ ou } 24$$

$$e) R_{in} = 0,25^2 \cdot R_L = 3,125 \, \Omega \quad \text{para } n = 0,24 \Rightarrow R_{in} = 0,24^2 \cdot 50 = 2,88 \, \Omega$$

$$f) \Gamma_{in} = \frac{0,24^2 - 1}{0,24^2 + 1} = -0,8911$$

$$g) R_{L_{dB}} = -20 \log |\Gamma_{in}| = -20 \log(0,8911) \approx 1 \, \text{dB}$$

$$h) P_s = 20 \, \text{dBm} \Rightarrow 10 \log \left(\frac{P_i}{1 \, \text{m}} \right) \Rightarrow P_i = 100 \cdot 10^{20/10} = 0,1 \, \text{W}$$

$$\Rightarrow R_L = 10 \log \left(\frac{P_i}{P_r} \right) \Rightarrow P_r = \frac{0,1}{10^{20/10}} \approx 79,43 \, \text{mW}$$

$$i) P_T = P_i - P_r = 20,57 \, \text{mW} \Rightarrow P_{T_{dBm}} = 10 \log \left(\frac{20,57 \, \text{m}}{1 \, \text{m}} \right) = 13,13 \, \text{dBm}$$

$$2) R_0 = 50 \Omega \\ R_L = 100 \Omega$$

$$a) R_{in} = n^2 R_L \Rightarrow n = \sqrt{\frac{50}{100}} = 0,7071$$

$$b) \Gamma_{in} = \frac{n^2 - 1}{n^2 + 1} = -1/3$$

$$c) R_{L/dB} = -20 \log(1/3) = 9,54 \text{ dB}$$

$$d) m_2 = 20 \Rightarrow m_1 = m_2 \cdot n = \frac{20}{\sqrt{100/3}} \approx 14$$

$$e) n \Rightarrow 14/20 = 0,7 \Rightarrow R_{in} = 0,7^2 R_L = 49 \Omega$$

$$f) \Gamma_{in} = \frac{0,7^2 - 1}{0,7^2 + 1} = -0,3423$$

$$g) R_{L/dB} = -20 \log(0,3423) = 9,32 \text{ dB}$$

$$h) P_S = -10 \text{ dBm} \Rightarrow P_i = 0,1 \text{ mW}$$

$$\Rightarrow P_r = \frac{P_i}{10^{\frac{R_{L/dB}}{20}}} = \frac{0,1 \text{ mW}}{10^{9,31/10}} = 11,71 \mu\text{W}$$

$$\Rightarrow P_{r/dBm} = 10 \log\left(\frac{11,71 \mu\text{W}}{1 \text{ mW}}\right) = -19,31 \text{ dBm}$$

$$i) P_T = P_i - P_r = 88,28 \mu\text{W} \Rightarrow P_{T/dBm} = 10 \log\left(\frac{88,28 \mu\text{W}}{1 \text{ mW}}\right) = -10,54 \text{ dBm}$$


3) L-matching network

$$f = 1 \text{ GHz}$$

$$R_s = 2 \Omega$$

$$R_L = 50 \Omega$$

$$a) |Q_s| = |Q_p| = \sqrt{\frac{R_L}{R_s} - 1} = \sqrt{\frac{50}{2} - 1} \approx 4,8989$$

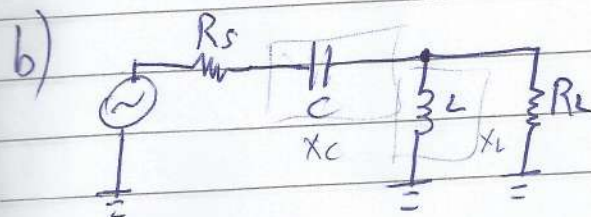

$$c) \frac{X_s}{R_s} = |Q_s| = 4,8989 \Rightarrow X_s = 2,48989 \approx 9,80 \Omega$$

$$\Rightarrow \frac{1}{\omega C} = X_s$$

$$\Rightarrow C = \frac{1}{2\pi \cdot 20^9 \cdot 9,80} = 26,24 \text{ pF}$$

$$d) |Q_p| = \frac{R_L}{X_p} \Rightarrow |X_p| = \frac{R_L}{4,8989} = 10,20$$

$$\Rightarrow \omega L = 10,20$$

$$\Rightarrow L = \frac{10,20}{2\pi \cdot 10^9} = 1,62 \text{ nH}$$

e) Series element: $C = 26,24 \text{ pF}$

f) Shunt element: $L = 1,62 \text{ nH}$

g) Igual item b)

$$h) \Delta f = \frac{f}{Q} = \frac{10^9}{4,8989} \approx 204 \text{ MHz}$$


4) L-matching network

$$f = 100 \text{ GHz}$$

$$R_s = 50 \Omega$$

$$R_L = 100 \Omega$$

$$a) |Q_s| = |Q_p| = \sqrt{\frac{100}{50} - 1} = 1$$

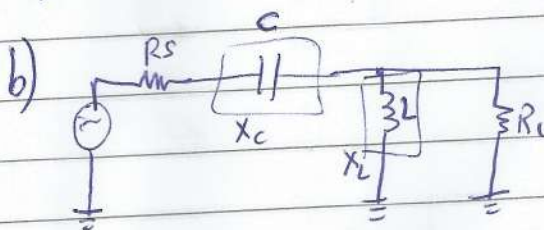

$$c) X_s = Q_s \cdot R_s = 50 \Omega$$

$$e) \text{Series element: } C = \frac{1}{\omega X_s} = \frac{1}{2\pi \cdot 100 \cdot 10^9 \cdot 50} = 31,83 \text{ fF}$$



$$d) X_p = \frac{R_L}{Q_p} = 100 \Omega$$

$$f) \text{Shunt element: } L = \frac{X_p}{\omega} = \frac{100}{2\pi \cdot 10^{11}} = 0,159 \text{ nH}$$

g) Igual item b)

$$h) \Delta f = \frac{f}{Q} = 100 \text{ GHz}$$

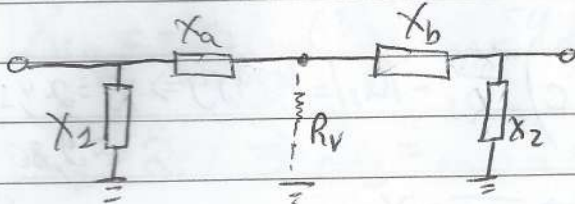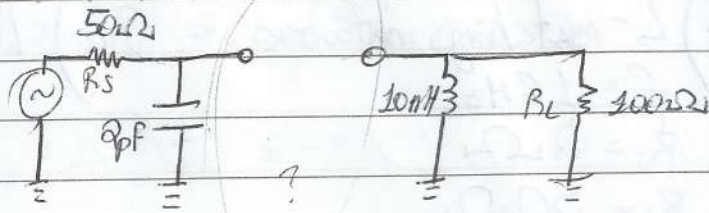5) π -network
 $f = 900 \text{ MHz}$
 $Q = 10$



$$\Rightarrow R_v = \frac{\max(R_s, R_L)}{Q^2 + 1}$$

$$= \frac{100}{101} = 0,99 \Omega$$

$$\Rightarrow Q_{\text{left}} = \sqrt{\frac{R_s}{R_v} - 1} = 7,03 = \frac{|X_a|}{R_v} = \frac{R_s}{|X_1|}$$

$$\Rightarrow |X_1| = \frac{R_s}{Q_{\text{left}}} = \frac{50}{7,03} = 7,1 \Omega \quad \Rightarrow |X_a| = R_v \cdot Q_{\text{left}} = 0,99 \cdot 7,03 = 6,96$$

$$|X_1| = \frac{1}{\omega C_1} \Rightarrow C_1 = \frac{1}{2\pi \cdot 900 \text{ M} \cdot 7,1} = 24,91 \text{ pF}$$

$$|X_a| = \omega L_a \Rightarrow L_a = \frac{6,96}{2\pi \cdot 900 \text{ M}} = 1,23 \text{ nH}$$

$$\Rightarrow Q_{\text{right}} = \sqrt{\frac{R_L}{R_v} - 1} \approx 10 = \frac{|X_b|}{R_v} = \frac{R_L}{|X_2|}$$

$$\Rightarrow |X_2| = \frac{R_L}{Q_{\text{right}}} = \frac{100}{10} = 10 \Omega \quad \Rightarrow |X_b| = R_v \cdot Q_{\text{right}} = 0,99 \cdot 10 = 9,9$$

$$|X_2| = \omega L_2 \Rightarrow L_2 = \frac{10}{2\pi \cdot 900 \text{ M}} = 1,77 \text{ nH}$$


$$|X_b| = \frac{1}{\omega C_b} \Rightarrow C_b = \frac{1}{2\pi \cdot 900 \text{ M} \cdot 9,9} = 17,86 \text{ pF}$$

$$\Rightarrow X_3 = X_a + X_b = 6,96 - 9,9 = -2,94$$


$$\Rightarrow C_3 = \frac{1}{2\pi \cdot 900 \text{ M} \cdot 2,94} = 60,15 \text{ pF}$$

$$\Rightarrow L_2 = \frac{L_2' \cdot 10 \text{ nH}}{10 \text{ nH} - L_2'} = 2,15 \text{ nH}$$

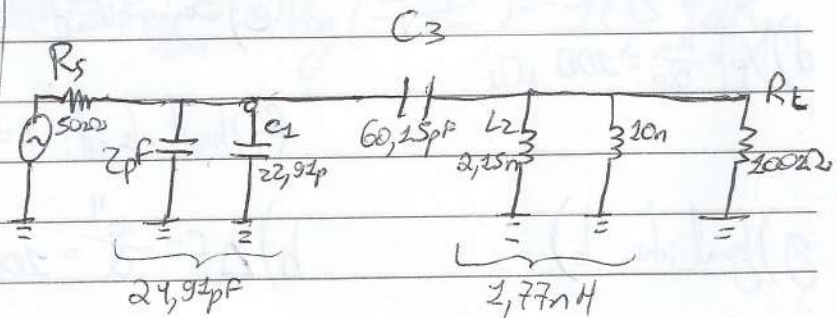
$$\Rightarrow C_2 = C_1 - 2 \text{ pF} = 22,91 \text{ pF}$$



6)

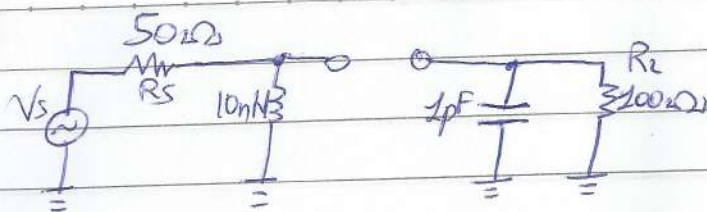

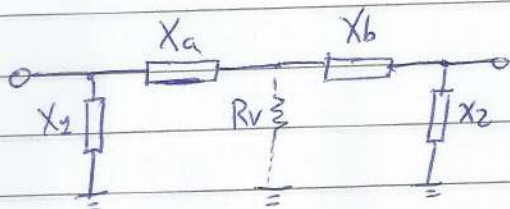Π -network
 $Q = 10$
 $f = 900 \text{ MHz}$



$$\Rightarrow R_v = \frac{\max(R_s, R_L)}{Q^2 + 1} = \frac{100}{101} = 0,99 \Omega$$

$$\Rightarrow Q_{\text{LEFT}} = \sqrt{\frac{R_s}{R_v} - 1} = 7,03 = \frac{|X_a|}{R_v} = \frac{R_s}{|X_1|}$$

$$\Rightarrow |X_1| = \frac{R_s}{Q_{\text{LEFT}}} = \frac{50}{7,03} = 7,12$$

$$\Rightarrow L_1' = \frac{X_1}{\omega} = \frac{7,12}{2\pi \cdot 900 \text{ M}} = 1,26 \text{ nH}$$

$$\Rightarrow |X_a| = R_v \cdot Q_{\text{LEFT}} = 0,99 \cdot 7,03 = 6,96$$

$$\Rightarrow C_a = \frac{1}{\omega X_a} = \frac{1}{2\pi \cdot 900 \text{ M} \cdot 6,96} = 25,42 \text{ pF}$$

$$\Rightarrow Q_{\text{RIGHT}} = \sqrt{\frac{R_L}{R_v} - 1} \approx 10 = \frac{|X_b|}{R_v} = \frac{R_L}{|X_2|}$$

$$\Rightarrow |X_2| = \frac{R_L}{Q_{\text{RIGHT}}} = \frac{100}{10} = 10$$

$$\Rightarrow C_2' = \frac{1}{\omega X_2} = \frac{1}{2\pi \cdot 900 \text{ M} \cdot 10} = 17,68 \text{ pF}$$

$$\Rightarrow |X_b| = R_v \cdot Q_{\text{RIGHT}} = 0,99 \cdot 10 = 9,9$$


$$\Rightarrow L_b = \frac{X_b}{\omega} = \frac{9,9}{2\pi \cdot 900 \text{ M}} = 1,75 \text{ nH}$$

$$\Rightarrow X_3 = X_a + X_b = -6,96 + 9,9 = 2,94$$

$$\Rightarrow L_3 = \frac{2,94}{2\pi \cdot 900 \text{ M}} = 0,52 \text{ nH}$$


$$\Rightarrow C_2 = C_2' - 1 \text{ p} = 16,68 \text{ pF}$$
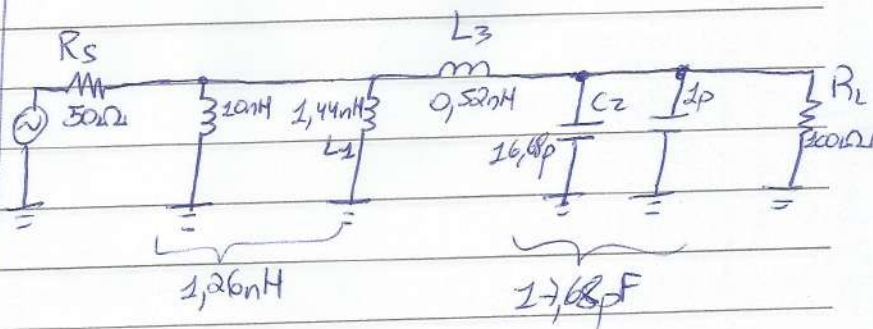
$$\Rightarrow L_2 = \frac{L_1' - 10 \text{ n}}{10 \text{ n} - L_1'} = 2,44 \text{ nH}$$



7) L-matching network

Equivalent a:

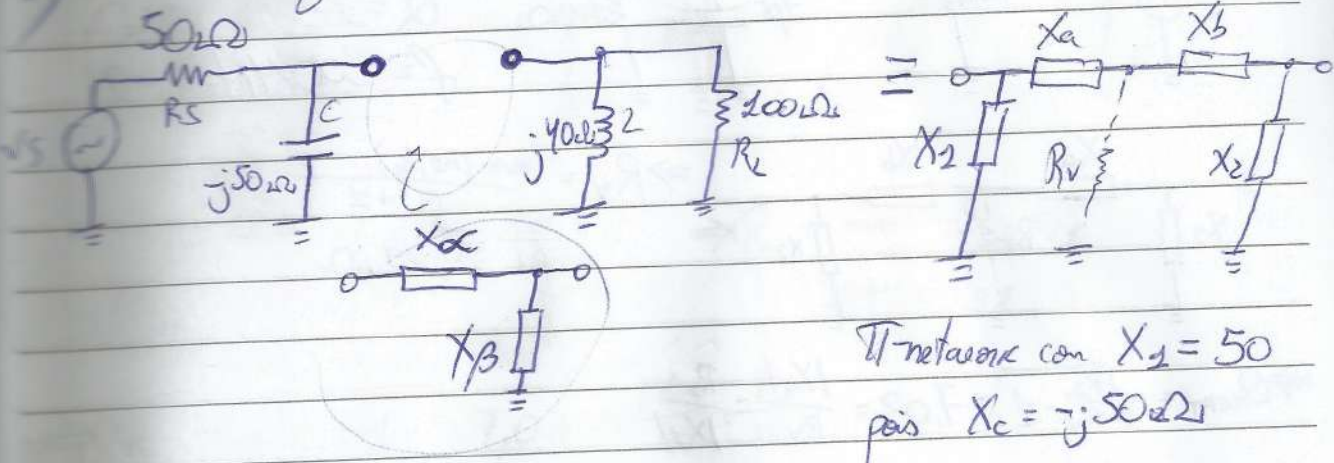

T-network with $X_2 = 50$
 plus $X_c = -j50\Omega$

Eqns:

$$\Rightarrow X_1 = 50 \Rightarrow Q_{LEFT} = \frac{R_S}{X_2} = \frac{50}{50} = 1$$

$$\Rightarrow R_V = \frac{R_S}{Q_{LEFT}^2 + 1} = \frac{50}{2} = 25$$


$$\Rightarrow Q_{RIGHT} = \sqrt{\frac{R_L}{R_V} - 1} = \sqrt{\frac{100}{25} - 1} = \sqrt{3} \approx 1,73$$

$$\Rightarrow X_a = Q_{LEFT} \cdot R_V = 25 \quad \Rightarrow X_1 = \frac{R_S}{Q_{LEFT}} = 50$$


$$\Rightarrow X_b = Q_{RIGHT} \cdot R_V = 1,73 \cdot 25 = 43,25 \quad \Rightarrow X_2 = \frac{R_S}{Q_{RIGHT}} = \frac{50}{1,73} = 28,9$$

$$\Rightarrow X_2 = 28,9 = \frac{X_3 \cdot 40}{X_2 + 40} \Rightarrow X_3 = \frac{40 \cdot X_2}{40 - X_2} = 204,14$$
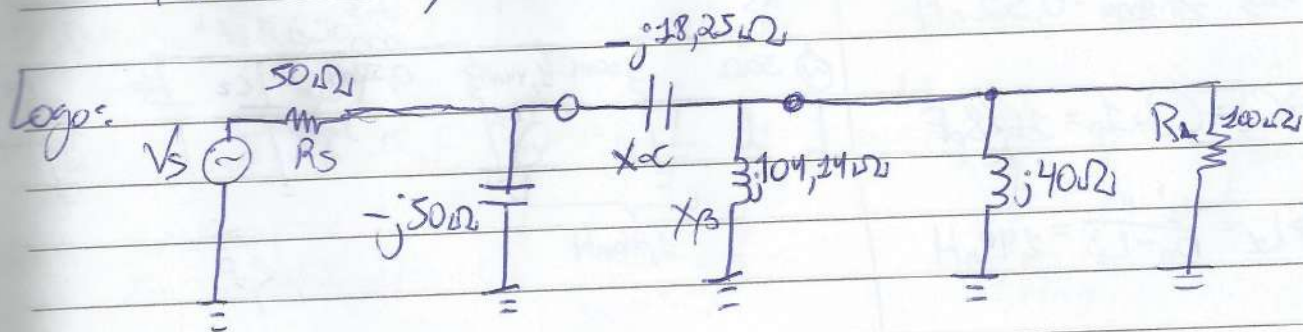
$$\Rightarrow X_a + X_b = 25 - 43,25 = -18,25$$



8) L-matching network

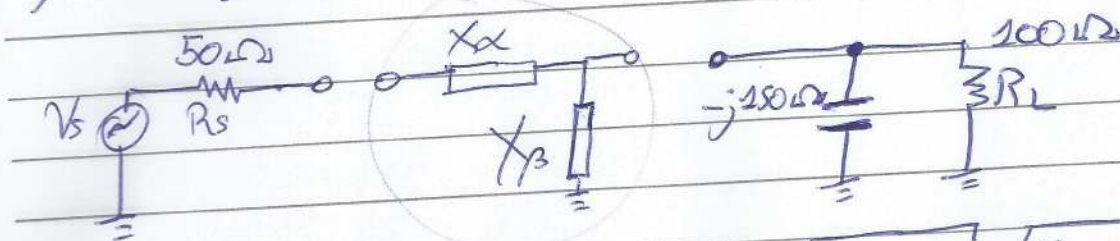

$$\Rightarrow X_p = X_p \parallel -j150 \Omega \quad \Rightarrow |Q_s| = |Q_p| = \sqrt{R_L/R_s - 1} = \sqrt{\frac{100}{50} - 1} = 1$$


$$\Rightarrow X_s = X_a$$

$$\Rightarrow X_p = \frac{R_L}{Q_p} = R_L = 100$$

$$\Rightarrow X_p = \frac{-j150 X_p}{-j150 - X_p} = 60 \quad (-60 \Omega \rightarrow \text{inductor})$$


$$\Rightarrow X_s = Q_s \cdot R_s = 50$$

Logo:

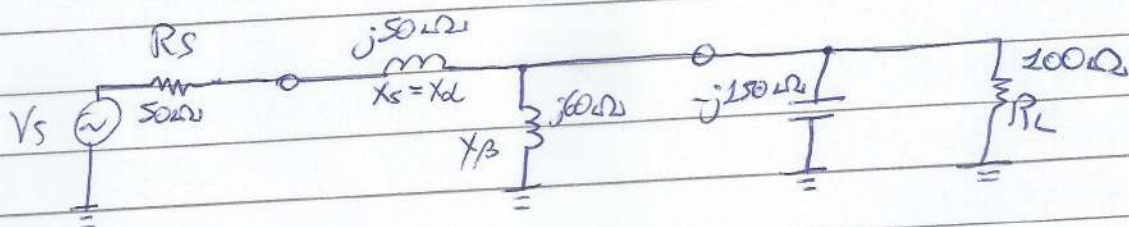

10) L-matching network
 $f = 100 \text{ GHz}$
 $R_s = 50 \Omega$
 $R_L = 200 \Omega$
 DC-blocking

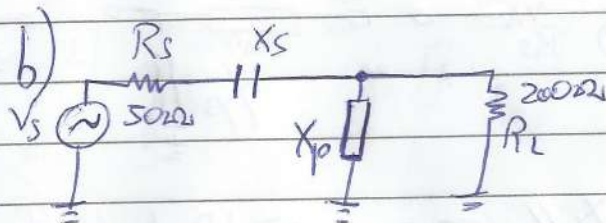a) $Q_s = \sqrt{\frac{R_L}{R_s} - 1} = \sqrt{\frac{200}{50} - 1} = \sqrt{3} \approx 1,73$



c) $X_s = R_s \cdot Q_s = 50 \cdot 1,73 = 86,5$

e) $C = \frac{1}{\omega X_s} = \frac{1}{2\pi \cdot 100 \cdot 86,5} \approx 18,4 \text{ fF}$


d) $X_p = \frac{R_L}{Q_p} = \frac{200}{1,73} = 115,61$

f) $L = \frac{X_p}{\omega} = \frac{115,61}{2\pi \cdot 100 \cdot 10^9} \approx 0,184 \text{ nH}$

g) Mesmo que item b)
 com X_p sendo indutor de $L = 0,184 \text{ nH}$

h) $\Delta f = \frac{f_0}{Q} = \frac{10^{11}}{1,73} \approx 57,86 \text{ GHz}$

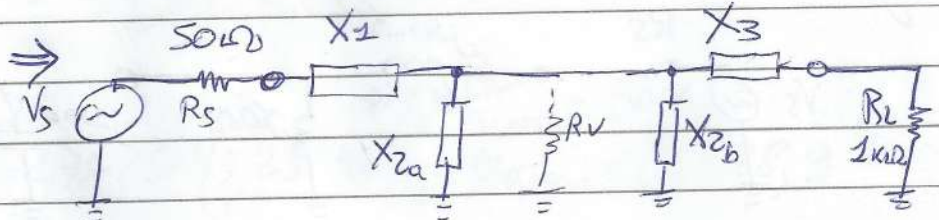21) T-network
 $R_s = 50 \Omega$
 $R_L = 1 \text{ k}\Omega$
 $Q = 15$



$\Rightarrow Q = \sqrt{\frac{R_V}{\min(R_s, R_L)} - 1} \Rightarrow R_V = (Q^2 + 1) \cdot [\min(R_s, R_L)] = 11 \cdot 300$

$\Rightarrow Q_1 = \sqrt{\frac{R_V}{R_s} - 1} = 15$

$\Rightarrow Q_2 = \sqrt{\frac{R_V}{R_L} - 1} = 3,21$

$\Rightarrow |X_1| = R_s \cdot Q_1 = 50 \cdot 15 = 750$

$\Rightarrow |X_2| = R_L \cdot Q_2 = 1 \text{ k} \cdot 3,21 = 3210$

$\Rightarrow |X_{2a}| = \frac{R_V}{Q_1} = \frac{11300}{15} = 753,33$

$\Rightarrow |X_{2b}| = \frac{R_V}{Q_2} = \frac{11300}{3,21} = 3520$

$\Rightarrow X_2 = X_{2a} \parallel X_{2b}$
 $= +j753 \parallel -j3520$
 $\approx +j958$

