


Circuitos RF

Setembro
2020

Gustavo Simas

$$Z_0 = 50 \Omega$$

S-parameters Matrix?

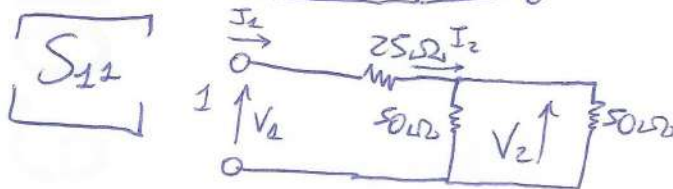

$$\Rightarrow Z_{in} = 25 + 50 // 50 = 50 \Omega$$

$$\Rightarrow S_{11} = \Gamma_{in} = \frac{Z_{in} - Z_0}{Z_{in} + Z_0}$$

$$= \frac{50 - 50}{50 + 50} = 0$$

$$S_{21} \Rightarrow V_1 = V_1^+ + V_1^- = V_1^+ (1 + S_{11})$$


$$\Rightarrow V_1^+ = \frac{V_1}{1 + S_{11}} = V_1 \Rightarrow V_1^- = 0$$

$$\Rightarrow V_1 = I_1 \cdot Z_{in} = 50 \cdot I_1 = 50 \cdot I_2 \Rightarrow I_1 = I_2$$

$$\Rightarrow V_2^- = V_2 = I_2 \cdot (50 // 50) = 25 \cdot I_2$$

$$\Rightarrow S_{21} = \frac{V_2^-}{V_1^+} = \frac{25}{50} = 0,5$$
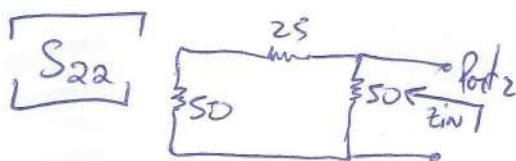
$$S_{12} \Rightarrow S_{12} = S_{21} \text{ (reciprocal network)}$$




$$\Rightarrow Z_{in} = 50 // (25 + 50)$$

$$= 30 \Omega$$

$$\Rightarrow S_{22} = \Gamma_{in} = \frac{30 - 50}{30 + 50} = -0,25$$
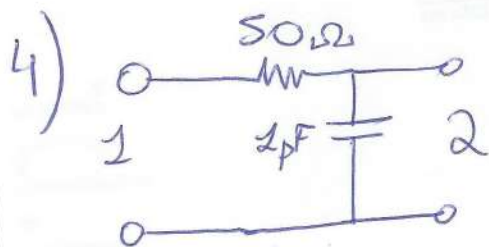
$$S \Rightarrow S = \begin{bmatrix} 0 & 0,5 \\ 0,5 & -0,25 \end{bmatrix}$$



Two port S parameters
1 GHz

$$50 \Omega = z_0$$

$$Z_c = \frac{1}{j\omega C} = \frac{1}{j \cdot 2\pi \cdot 10^9 \cdot 2 \cdot 10^{-12}}$$

$$\Rightarrow Z_c = \frac{-j}{2\pi \cdot 10^9 \cdot 2 \cdot 10^{-12}} \approx -j159,15 \Omega$$

$$\Rightarrow Z_{in} = 50 + (Z_c \parallel 50)$$

$$= 95,51 - j24,3 \Omega$$

$$\Rightarrow \underline{S_{11}} = \Gamma_{in} = \frac{Z_{in} - z_0}{Z_{in} + z_0} = 0,3193 - j0,0669$$

$$\underline{S_{21}} \Rightarrow V_1^+ = \frac{V_1}{1 + S_{11}} = (0,756 + j0,038) \cdot V_1$$

$$\underline{S_{12}} \Rightarrow V_2 = I_1 \cdot Z_{in} = I_1 \cdot (95,51 - j24,3) \quad I_1 = I_2$$

$$\Rightarrow V_2^- = V_2 = I_2 \cdot (50 \parallel Z_c) = I_2 \cdot (45,51 - j24,3)$$

$$\Rightarrow S_{21} \Rightarrow \frac{V_2^-}{V_1^+} = 2 + j0,314$$


$$S_{21} = S_{12} = \frac{V_2^-}{V_1^+} = 0,638 - j0,13$$

$$\underline{S_{22}} \Rightarrow Z_{in} = (50 + 50) \parallel Z_c = 71,69 - j45,05 \Omega$$

$$\Rightarrow S_{22} = \Gamma_{in} = \frac{Z_{in} - z_0}{Z_{in} + z_0} = 0,277 - j0,267$$

$$S = \begin{bmatrix} 0,3193 - j0,0669 & 0,638 - j0,13 \\ 0,638 - j0,13 & 0,277 - j0,267 \end{bmatrix}$$

5)

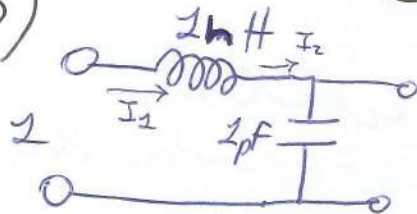

Two port 50Ω
S-parameters $f=16\text{Hz}$

$$\Rightarrow Z_L = j\omega L = j \cdot 2\pi \cdot 10^9 \cdot 2 \cdot 10^{-3} = j6,28\Omega$$

$$\Rightarrow Z_C = \frac{j}{\omega C} = j \cdot \frac{1}{2\pi \cdot 10^9 \cdot 2 \cdot 10^{-12}} = j159,15\Omega$$

$$\boxed{S_{11}} \Rightarrow Z_{in} = Z_L + (Z_C // Z_0) = j6,28 + (50 // -j159,15) = 45,51 + j8,02\Omega$$

$$\Rightarrow S_{11} = \Gamma_{in} = \frac{Z_{in} - Z_0}{Z_{in} + Z_0} = \boxed{-0,0397 + j0,0872}$$

$$\boxed{S_{21}} \Rightarrow V_1^+ = \frac{V_1}{1 + S_{11}} = (1,03 + j0,094)V_2$$

$$\Rightarrow V_1 = I_1 \cdot Z_{in} = I_{in} \cdot (45,51 - j8,02)$$

$$\Rightarrow V_1^+ = (45,51 - j8,02) \cdot (1,03 + j0,094) \cdot I_1 = (47,75 - j4) \cdot I_1$$

$$\Rightarrow V_2^- = I_2 \cdot (50 // Z_C) = I_1 \cdot (45,51 - j14,3)$$

$$\Rightarrow S_{21} = S_{12} = \frac{V_2^-}{V_1^+} = \boxed{0,971 - j0,218}$$


$$\boxed{S_{22}} \Rightarrow Z_{in} = (50 + Z_L) // Z_C = 48,96 - j9,47\Omega$$

$$\Rightarrow S_{22} = \Gamma_{in} = \boxed{-0,00136 - j0,0958}$$

$$S = \begin{bmatrix} 0,959 \angle -115^\circ & 0,995 \angle -12,64^\circ \\ 0,995 \angle -12,64^\circ & 0,0958 \angle -90,81^\circ \end{bmatrix}$$

www.unesporte.org.br

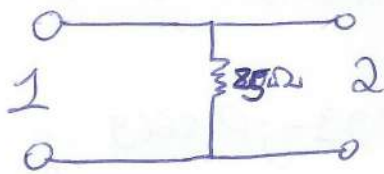6) Two port S parameters
Shunt 25Ω resistor
 $Z_0 = 50\Omega$



$$\boxed{S_{11}} \Rightarrow S_{11} = \frac{Y_0 - Y_{in}}{Y_0 + Y_{in}}$$

$$\Rightarrow S_{11} = \frac{-Y}{2Y_0 + Y} = \frac{-0,04}{2 \cdot 0,02 + 0,04} = -0,5$$

$$Y = \frac{1}{Z} = \frac{1}{25} = 0,04 \text{ A/V}$$

$$\Rightarrow S_{11} = S_{22}$$


$$Y_0 = \frac{1}{Z_0} = \frac{1}{50} = 0,02 \text{ S}$$

$$\boxed{S_{21}} \Rightarrow S_{21} = \frac{2Y_0}{Y + 2Y_0} = \frac{2 \cdot 0,02}{0,04 + 2 \cdot 0,02} = 0,5$$

$$S_{21} = S_{12}$$

$$S = \begin{bmatrix} -0,5 & 0,5 \\ 0,5 & -0,5 \end{bmatrix}$$

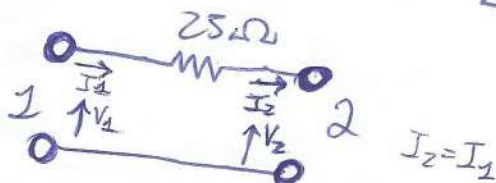7) Two port S parameters
 Series 25Ω resistor
 $Z_0 = 100\Omega$



$$S_{11} \Rightarrow Z_{in} = 25 + 100 = 125\Omega$$

$$\Rightarrow S_{11} = \Gamma_{in} = \frac{Z_{in} - Z_0}{Z_{in} + Z_0} = \frac{125 - 100}{125 + 100} = 0,11$$

$$S_{22} \Rightarrow V_1 = V_1^+ + V_1^- = V_1^+ (1 + S_{22})$$

$$\Rightarrow V_1^+ = \frac{V_1}{(1 + S_{22})} = 0,9 V_1$$

$$\Rightarrow V_1 = I_1 \cdot Z_{in} = 125 I_1$$

$$\Rightarrow V_1^+ = 112,5 \cdot I_1$$

$$\Rightarrow V_2^- = V_2 = I_2 \cdot 100 = 100 \cdot I_2$$

$$\Rightarrow S_{21} = \frac{V_2^-}{V_1^+} = \frac{100}{112,5} = 0,89$$

$$\Rightarrow S_{21} = S_{12}$$

(rede recíproca)

$$S_{22} \Rightarrow Z_{in} = 25 + 100 = 125$$

$$\Rightarrow S_{22} = \Gamma_{in} = \frac{Z_{in} - Z_0}{Z_{in} + Z_0} = 0,11$$


(rede simétrica)

Logo

$$S = \begin{bmatrix} 0,11 & 0,89 \\ 0,89 & 0,11 \end{bmatrix}$$

8) Two port Π -network

$$Z_0 = 50 \Omega$$

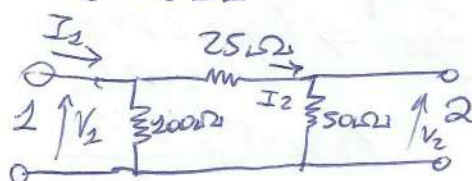

$$\boxed{S_{11}}$$

$$\Rightarrow Z_{in} = 100 // (25 + (50 // 100)) = 33,33 \Omega$$

$$\Rightarrow S_{11} = \Gamma_{in} = \frac{Z_{in} - Z_0}{Z_{in} + Z_0} = -0,2$$

$$\boxed{S_{21}} \Rightarrow V_1^+ = \frac{V_2}{1 + S_{11}} = \frac{1}{1 - 0,2} \cdot V_2 = 1,25 \cdot V_2$$

$$\Rightarrow V_1 = I_1 \cdot Z_{in} = 33,33 \cdot I_1$$

$$\Rightarrow V_1^+ = 1,25 \cdot 33,33 \cdot I_1 = 41,66 \cdot I_1$$

$$\Rightarrow V_1^+ = I_2 \cdot 1,25 \cdot (25 + 50 // 100) = 62,5 \cdot I_2$$

$$\Rightarrow V_2^- = V_2 = I_2 \cdot (50 // 100) = 25 \cdot I_2$$

$$\Rightarrow S_{21} = \frac{V_2^-}{V_1^+} = \frac{25 \cdot I_2}{62,5 \cdot I_2} = 0,4$$

$$S_{21} = S_{12} \text{ rede recíproca}$$


$$\boxed{S_{22}} \Rightarrow Z_{in} = 50 // (25 + (50 // 100)) = 26,92 \Omega$$

$$\Rightarrow S_{22} = \Gamma_{in} = \frac{26,92 - 50}{26,92 + 50} = -0,3$$

Logo

$$S = \begin{bmatrix} -0,2 & 0,4 \\ 0,4 & -0,3 \end{bmatrix}$$

g) Two port T-network

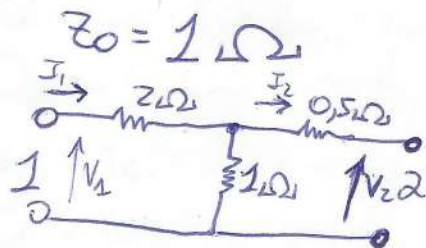

$$\boxed{S_{11}} \Rightarrow Z_{in} = 2 + (1 // (0,5 + 1)) = 2,6 \Omega$$

$$\Rightarrow S_{11} = \Gamma_{in} = \frac{Z_{in} - Z_0}{Z_{in} + Z_0} = \frac{2,6 - 1}{2,6 + 1} = \frac{1,6}{3,6} = \frac{4}{9}$$

$$\approx 0,44$$

$$\boxed{S_{21}} \Rightarrow V_2^+ = \frac{V_2}{1 + S_{11}} = 0,69 \cdot V_2$$

$$\Rightarrow V_2 = I_2 \cdot Z_{in} = 2,6 \cdot I_2$$

$$\Rightarrow V_2^+ = 2,6 \cdot 0,69 \cdot I_2 \approx 1,8 \cdot I_2$$

$$\Rightarrow I_2 = I_1 \cdot \frac{1}{2 + 0,5 + 1} = 0,4 \cdot I_1$$

$$\Rightarrow V_2^- = V_2 = Z_0 \cdot I_2 = I_2$$

$$\Rightarrow S_{21} = \frac{V_2^-}{V_2^+} = \frac{0,4 \cdot I_1}{1,8 \cdot I_1}$$

$$= \frac{2}{9}$$

$$\approx 0,22$$

$$S_{21} = S_{12} \quad \text{reciprocal}$$

$$\boxed{S_{22}} \Rightarrow Z_{in} = 0,5 + (1 // (2 + 1)) = 1,25 \Omega$$

$$\Rightarrow S_{22} = \Gamma_{in} = \frac{1,25 - 1}{1,25 + 1} = \frac{0,25}{2,25} = \frac{1}{9} \approx 0,11$$


Logo

$$S = \begin{bmatrix} 0,44 & 0,22 \\ 0,22 & 0,11 \end{bmatrix}$$

B) $S = \begin{bmatrix} 0,5 + j0,5 & 0,95 + j0,25 \\ 0,15 - j0,05 & 0,5 - j0,5 \end{bmatrix}$

$Z_0 = 50 \Omega$

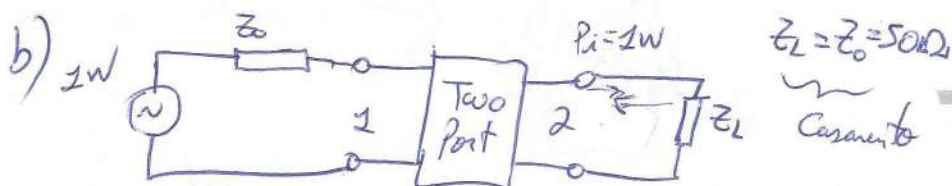a) Não é recíproco, pois $S_{12} \neq S_{21}$



$RL_{dB} = -20 \log |S_{11}| \Rightarrow |S_{11}| = \sqrt{\text{Re}(S_{11})^2 + \text{Im}(S_{11})^2}$
 \downarrow
 Return Loss
 $= \sqrt{0,5^2 + 0,5^2}$
 $= 0,7071$

$\Rightarrow RL_{dB} = -20 \log(0,7071) \approx 3,01 \text{ dB}$

$\Rightarrow RL_{dB} = 10 \log \frac{P_i}{P_r} = 3,01 \Rightarrow \frac{P_i}{P_r} = 10^{3,01/10} = 2$

$\Rightarrow P_r = \frac{1}{2} = 0,5 \text{ W}$

Logo $P_L = 0,5 \text{ W}$

c) Máxima Transferência de Potência

$\Rightarrow RL_{dB} = 0 = 10 \log \left| \frac{1}{\rho^2} \right|$

$\Rightarrow \rho^2 = 1$

$\Rightarrow \rho = 1$

13) c) ^{CONTINUADO} $\Rightarrow S_{11} + \frac{\Gamma_L \cdot S_{12} \cdot S_{21}}{(1 - \Gamma_L \cdot S_{22})} = \rho = 1$

$$\Rightarrow \Gamma_L \cdot S_{12} \cdot S_{21} = (1 - S_{11}) \cdot (1 - \Gamma_L \cdot S_{22})$$

$$\Rightarrow \Gamma_L \cdot S_{12} \cdot S_{21} = 1 - \Gamma_L \cdot S_{22} - S_{11} + \Gamma_L \cdot S_{11} \cdot S_{22}$$

$$\Rightarrow \Gamma_L \cdot (S_{12} \cdot S_{21} + S_{22} - S_{11} \cdot S_{22}) = 1 - S_{11}$$

$$\Rightarrow \Gamma_L = \frac{(1 - S_{11})}{(S_{12} \cdot S_{21} + S_{22} - S_{11} \cdot S_{22})}$$

$$= \frac{(1 - 0,5j0,5)}{[(10,95 + j0,25) \cdot (0,15 - j0,05) + 0,5 - j0,5 - (0,5 + j0,5) \cdot (0,5 - j0,5)]}$$

$$\Rightarrow \Gamma_L = 1,17 + j0,62$$

$$= 1,33 \angle 28,09^\circ$$

Two port
14) $Z_0 = 50 \Omega$

$$S_{11} = 0,3 - j0,4$$

$$S_{21} = 0,5$$

Se
a) Recíproca
então

$$S_{12} = S_{21} = 0,5$$

b) Sem perdas se $|S_{11}|^2 + |S_{21}|^2 = 1$ (I)

$$|S_{12}|^2 + |S_{22}|^2 = 1$$
 (II)

Condição (I) confere pois $\sqrt{0,3^2 + 0,4^2} + \sqrt{0,5^2} = 1$

Se $S_{12} = 0,5$, então S_{22} deve ser 0,5 para que seja sem perdas.

c) $Z_L = Z_0 = 50 \Omega$ (casamento)

$$P_i = 0 \text{ dBm} = 1 \text{ mW}$$

$$\Rightarrow RL_{dB} = -20 \log |S_{11}| = -20 \log (0,5) = 6,02 \text{ dB}$$

$$\Rightarrow RL_{dB} = 10 \log \left(\frac{P_i}{P_r} \right) \Rightarrow \frac{P_i}{P_r} = 10^{\frac{6,02}{10}} = 4$$

$$\Rightarrow P_r = \frac{P_i}{4} = 0,25 \text{ mW}$$

$$\Rightarrow P_L = 0,75 \text{ mW}$$

$$15) S = \begin{bmatrix} 0,25 & 0 \\ 1,2 & 0,5 \end{bmatrix}$$


$$Z_0 = 50 \Omega$$

$$Z_G = 50 \Omega$$

$$P_s = 1 \text{ mW}$$

$$Z_L = 25 \Omega$$

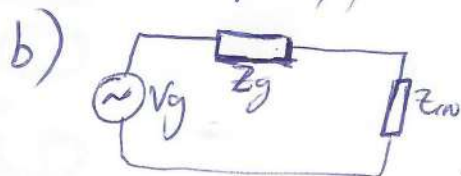a) Não recíproca, pois $S_{12} \neq S_{21}$



$$\Rightarrow \Gamma_{in} = S_{11} + \frac{\Gamma_L \cdot S_{12} \cdot S_{21}}{1 - \Gamma_L \cdot S_{22}}$$

$$= S_{11} = 0,25$$

$$\Rightarrow \Gamma_{in} = \frac{Z_{in} - Z_0}{Z_{in} + Z_0} \Rightarrow 0,25 \cdot Z_{in} + 0,25 \cdot Z_0 = Z_{in} - Z_0$$

$$\Rightarrow Z_{in} = \frac{1,25 \cdot 50}{0,75} = 83,33 \Omega$$

$$\Rightarrow P_s = \frac{V_g^2}{Z} \Rightarrow V_g = \sqrt{P_s \cdot Z}$$

$$= \sqrt{0,001 \cdot (50 + 83,33)}$$

$$\approx 0,365 \text{ V}$$

c) $R_{LdB} = -20 \log |\Gamma_{in}| = -20 \log (0,25) = 12,04 \text{ dB}$

$$= 10 \log \left(\frac{P_i}{P_r} \right) \Rightarrow P_i = P_s \cdot \frac{Z_{in}}{Z_{in} + Z_G} = 0,001 \cdot \frac{83,33}{83,33 + 50}$$

$$= 0,625 \text{ mW}$$

$$\Rightarrow P_r = \frac{0,625}{10^{(12,04/10)}} = 39,06 \mu\text{W}$$

$$15) d) \delta_s = (1 - S_{11})(1 - S_{22}) - S_{12} \cdot S_{21} \\ = (1 - 0,25) \cdot (1 - 0,5) = 0,375$$

$$Z_{11} = [(1 + S_{11})(1 - S_{22}) + S_{12} \cdot S_{21}] / \delta_s \\ = (2 + 0,25)(1 - 0,5) / 0,375 \approx 1,67$$

$$Z_{12} = 2 \cdot S_{12} / \delta_s = 2 \cdot 0 / 0,375 = 0$$

$$Z_{21} = 2 \cdot S_{21} / \delta_s = 2 \cdot 1,2 / 0,375 = 6,4$$

$$Z_{22} = [(1 - S_{11})(1 + S_{22}) + S_{12} \cdot S_{21}] / \delta_s \\ = [(1 - 0,25)(1 + 0,5)] / 0,375 = 3$$

↓
Parâmetros normalizados por $Z_0 = 50 \Omega$

Parâmetros atuais = $Z'_{11} = z_{11} \cdot Z_0 = 83,5$


$$Z'_{12} = z_{12} \cdot Z_0 = 0$$

$$Z'_{21} = z_{21} \cdot Z_0 = 320$$

$$Z'_{22} = z_{22} \cdot Z_0 = 150$$

$$Z = \begin{bmatrix} 83,5 & 0 \\ 320 & 150 \end{bmatrix}$$

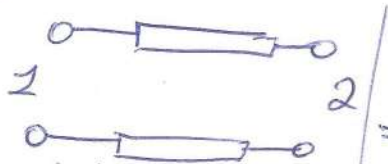17) Transmission Line comprimento $l = \frac{\lambda}{4}$



β : constante de propagação
 $\beta = \frac{2\pi}{\lambda}$

$$\begin{aligned} \Rightarrow A &= \cos(\beta l) \\ \Rightarrow B &= j \cdot Z_0 \cdot \sin(\beta l) \\ \Rightarrow C &= j \cdot Y_0 \cdot \sin(\beta l) \\ \Rightarrow D &= \cos(\beta l) \end{aligned}$$

$$\begin{aligned} \Rightarrow A &= \cos(\beta l) = \cos\left(\frac{2\pi}{\lambda} \cdot \frac{\lambda}{4}\right) = \cos\left(\frac{\pi}{2}\right) = 0 \\ \Rightarrow B &= j \cdot Z_0 \cdot \sin(\beta l) = j \cdot Z_0 \cdot \sin\left(\frac{\pi}{2}\right) = j \cdot Z_0 \\ \Rightarrow C &= j \cdot Y_0 \cdot \sin(\beta l) = j \cdot Y_0 \\ \Rightarrow D &= \cos(\beta l) = 0 \end{aligned}$$

$$\Rightarrow \Delta = A + B/Z_0 + C \cdot Z_0 + D = j \cdot 2$$


$$\Rightarrow S_{11} = \frac{A + B/Z_0 - C \cdot Z_0 - D}{\Delta} = 0 \quad \Rightarrow S_{21} = \frac{2}{\Delta} = -j$$

$$\Rightarrow S_{22} = \frac{-A + B/Z_0 - C \cdot Z_0 + D}{\Delta} = 0 \quad \Rightarrow S_{12} = \frac{2(AD - BC)}{\Delta} = -j$$

$$S = \begin{bmatrix} 0 & -j \\ -j & 0 \end{bmatrix}$$

rede recíproca
e simétrica

18) Two Port

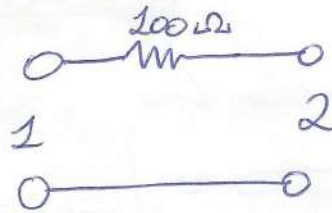

$$Z_0 = 50 \Omega$$

$$\begin{aligned} a) \Rightarrow A &= 1 & B &= Z = 100 \Omega \\ C &= 0 & D &= 1 \end{aligned}$$

$$\Rightarrow \Delta = A + B/Z_0 + C \cdot Z_0 + D = 4$$

$$\Rightarrow S_{11} = \frac{A + B/Z_0 - C \cdot Z_0 - D}{\Delta} = 0,5 \quad \left| \quad \Rightarrow S_{21} = \frac{2}{\Delta} = 0,5 \right.$$



$$\Rightarrow S_{12} = \frac{2 \cdot (AD - BC)}{\Delta} = 0,5 \quad \left| \quad \Rightarrow S_{22} = \frac{-A + B/Z_0 - (C \cdot Z_0 + D)}{\Delta} = 0,5 \right.$$

$$S = \begin{bmatrix} 0,5 & 0,5 \\ 0,5 & 0,5 \end{bmatrix}$$

$$b) \begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} 1 & 100 \\ 0 & 1 \end{bmatrix}$$

19) Two port

$$Z_0 = 50 \Omega$$

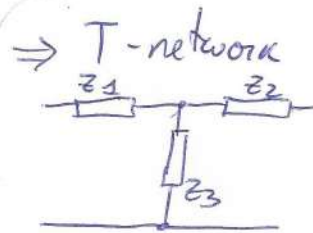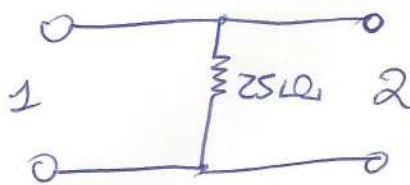

Pela tabela de parâmetros ABCD temos:

Com $Z_1 = Z_2 = 0$

$$\Rightarrow A = 1 \quad \Rightarrow B = 0$$

$$\Rightarrow C = Y = \frac{1}{Z} = \frac{1}{25} = 0,04 \quad \Rightarrow D = 1$$

$$\Rightarrow \Delta = A + B/Z_0 + C \cdot Z_0 + D = 4$$

$$\Rightarrow S_{11} = \frac{A + \frac{B}{Z_0} - C \cdot Z_0 - D}{\Delta} = -0,5 \quad \Rightarrow S_{21} = \frac{2}{\Delta} = 0,5$$

$$\Rightarrow S_{12} = \frac{2 \cdot (AD - BC)}{\Delta} = 0,5$$

$$\Rightarrow S_{22} = \frac{-A + \frac{B}{Z_0} - C \cdot Z_0 + D}{\Delta} = -0,5$$

$$\text{Logo } S = \begin{bmatrix} -0,5 & 0,5 \\ 0,5 & -0,5 \end{bmatrix}$$

$$b) \begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} 1 & 0 \\ 0,04 & 1 \end{bmatrix}$$

22) Atenuador 50Ω , 10dB $S_{11}=S_{22}=0$
 $Z_0=75\Omega$
 I_L

a) Referência 50Ω : $-10\text{dB} = 20\log(S_{21})$
 $\Rightarrow S_{21}=S_{12}=10^{\frac{-10}{20}} = 0,316$

$$S = \begin{bmatrix} 0 & 0,316 \\ 0,316 & 0 \end{bmatrix}$$

Referência 75Ω

$$\Rightarrow \Gamma_{75} = \frac{75-50}{75+50} = 0,2$$

$$\Rightarrow {}^{75}S = \begin{bmatrix} {}^{50}S_{11}-\Gamma_{75} & {}^{50}S_{12} \\ {}^{50}S_{21} & {}^{50}S_{22}-\Gamma_{75} \end{bmatrix}$$

$$= \begin{bmatrix} 1-\Gamma_{75} \cdot {}^{50}S_{11} & \Gamma_{75} \cdot {}^{50}S_{12} \\ -\Gamma_{75} \cdot {}^{50}S_{21} & 1-\Gamma_{75} \cdot {}^{50}S_{22} \end{bmatrix}$$

$$= \begin{bmatrix} -0,2 & 0,316 \\ 0,316 & -0,2 \end{bmatrix} \cdot \begin{bmatrix} 1 & -0,0632 \\ 0,0632 & 1 \end{bmatrix}$$

$$= \begin{bmatrix} -0,22 & 0,32884 \\ 0,3288 & -0,22 \end{bmatrix}$$

Logo, coeficiente de transmissão: $S_{21} = 0,328$

$$\begin{aligned} 22) b) \quad 75 \text{ IL}_{\text{dB}} &= 10 \log \left(\frac{1}{|75 S_{21}|^2} \right) \\ &= 10 \log \left(\frac{1}{0,328} \right) = 4,84 \text{ dB} \end{aligned}$$

$$\begin{aligned} c) \text{ Carga casada } Z_L &= Z_0^* = 75 \Omega \\ \Rightarrow \Gamma_{in} = S_{11} &= -0,22 \end{aligned}$$